

School of Electronic and Communications Engineering





Lecture 3a.
Noise Tutorial

Gray, P.R. & Meyer, R.G.,
Analysis and Design of Analog Integrated Circuits.
(3rd Edition), Wiley (1992) [621.3815](#)

DT021/4 Electronic Systems – Lecture 3a: Noise Tutorial 1.

School of Electronic and Communications Engineering

Noise Sources (resume)

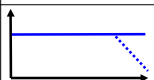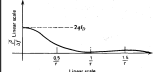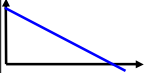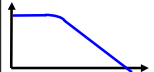Noise	Origin	Expression	Spectral density
thermal noise (Gaussian)	random fluctuations of velocity	$\overline{i_t^2} = 4kT\Delta f / R$	
shot noise (Gaussian)	due to DC current through p-n junction	$\overline{i_s^2} = 2qI_D \cdot \Delta f$	
flicker noise	traps in crystal lattice (semiconductors, carbon, etc.)	$\overline{i_f^2} = K_1 \frac{I_{DC}^\alpha}{f^\beta} \cdot \Delta f$	
burst noise	heavy-metal ions contamination. (gold, etc.)	$\overline{i_b^2} = K_2 \frac{I^c}{1 + (f / f_c)^2} \cdot \Delta f$	
avalanche noise	due to avalanche breakdown in zener diodes		

DT021/4 Electronic Systems – Lecture 3a: Noise Tutorial 2.

School of Electronic and Communications Engineering

Exam Questions

a) Noise Sources and Properties. PDF-PSD [5-7 marks]

b) Noise analysis: OpAmp – BJT [12-15 marks]

c) Noise Figure. [5-7 marks]

DT021/4 Electronic Systems – Lecture 3a: Noise Tutorial 3.

School of Electronic and Communications Engineering

Invariants

- The mean-square value can be separated into a **time-invariant** part and a **time-varying** part.
- The **time-invariant** or **static** part is the square of the *signal average* or *mean value*,

$$\mu_x \equiv \lim_{T \rightarrow \infty} \frac{1}{T} \int_0^T x(t) dt$$
- The time-varying or dynamic part of the mean-square value is the **signal variance**, which is defined as the mean-square value of $x(t)$ about its mean value,


$$\sigma_x^2 \equiv \lim_{T \rightarrow \infty} \frac{1}{T} \int_0^T [x(t) - \mu_x]^2 dt$$

It follows that

$$\psi_x^2 = \mu_x^2 + \sigma_x^2$$

The positive square root of the variance is the **standard deviation**.

DT021/4 Electronic Systems – Lecture 3a: Noise Tutorial 4.


School of Electronic and Communications Engineering  **Probability Density Function**

- The amplitude distribution of a random signal is described by the *probability density function* (PDF), $p(x)$, defined as


$$p(x) \equiv \lim_{\Delta x \rightarrow 0} \frac{\text{Prob}[x < x(t) < x + \Delta x]}{\Delta x} = \lim_{\Delta x \rightarrow 0} \frac{1}{\Delta x} \left[\lim_{T \rightarrow \infty} \frac{T_x}{T} \right]$$

- where T_x is the amount of time in which $x(t)$ falls inside the amplitude interval from x to $x + \Delta x$.
- Therefore, the PDF gives the probability that the signal amplitude at any arbitrary moment lies inside a given amplitude range.

DT021/4 Electronic Systems – Lecture 3a: Noise Tutorial 5.

School of Electronic and Communications Engineering 

DT021/4 Electronic Systems – Lecture 3a: Noise Tutorial 6.


School of Electronic and Communications Engineering  **Power Spectral Density (PSD)**

- The *power spectral density* (PSD) consider the distribution of noise power in different frequency bands.
- The PSD of a random signal $x(t)$ is

$$G_{xx}(f) = \lim_{\Delta f \rightarrow 0} \frac{\psi_x^2(f, \Delta f)}{\Delta f} = \lim_{\Delta f \rightarrow 0} \frac{1}{\Delta f} \left[\lim_{T \rightarrow \infty} \frac{1}{T} x^2(t, f, \Delta f) dt \right]$$

- where $\psi_x^2(f, \Delta f)$ is the signal power in the frequency band from f to $f + \Delta f$ and $x(t, f, \Delta f)$ is that part of $x(t)$ contributing to power in the frequency band from f to $f + \Delta f$.

DT021/4 Electronic Systems – Lecture 3a: Noise Tutorial 7.

School of Electronic and Communications Engineering 

DT021/4 Electronic Systems – Lecture 3a: Noise Tutorial 8.

Gaussian (normal) PDF

- Electronic noise has a **Gaussian** PDF because it results from a large number of random, independent events.
- This means that its PDF is bell-shaped and follows the equation:

$$p(x) = \frac{1}{\sigma_x \sqrt{2\pi}} e^{-\frac{(x-\mu_x)^2}{2\sigma_x^2}} = \frac{1}{\sigma_x \sqrt{2\pi}} e^{-\frac{x^2}{2\sigma_x^2}}$$

Ordinates are the probability density of a specific x-value
(in σ -units !!!).

DT021/4 Electronic Systems – Lecture 3a: Noise Tutorial 9.

School of Electronic and Communications Engineering

D.T.T.

DT021/4 Electronic Systems – Lecture 3a: Noise Tutorial 10.

PDF Tutorial

- The PDF function of the thermal noise is given by the following expression:

$$p(x) = \frac{1}{\sigma_x \sqrt{2\pi}} e^{-\frac{x^2}{2\sigma_x^2}}$$

- Assuming a room temperature $T = 300$ K calculate:
- (i) rms value of noise voltage of 10 k Ω resistor over the bandwidth 10 MHz;
- (ii) the probability of 80 μ V noise voltage.

DT021/4 Electronic Systems – Lecture 3a: Noise Tutorial 11.

School of Electronic and Communications Engineering

D.T.T.

DT021/4 Electronic Systems – Lecture 3a: Noise Tutorial 12.

School of Electronic and Communications Engineering

Signal to Noise ratio

- The common parameter to characterize signals is their power.
- In all practical systems the signal always coexists with noise.
- Therefore it can be described by very important parameter Signal-to-Noise Ratio (SNR or S/N):

$$SNR(dB) \equiv 10 \cdot \lg \left(\frac{\text{Signal Power}}{\text{Noise Power}} \right)$$

DT021/4 Electronic Systems – Lecture 3a: Noise Tutorial 17.

School of Electronic and Communications Engineering

DT021/4 Electronic Systems – Lecture 3a: Noise Tutorial 18.

School of Electronic and Communications Engineering

Noise Figure

- The *noise figure (F)* specifies the noise performance of a circuit or a device.
- The definition of the noise figure of a circuit is

$$F \equiv \frac{\text{Input } S / N \text{ Ratio}}{\text{Output } S / N \text{ Ratio}}$$

- ❖ Its *disadvantage* is that it is limited to situations where the source impedance is *resistive*
- ❖ However, it is widely used as a measure of noise performance in communication systems where the source impedance is often resistive.

DT021/4 Electronic Systems – Lecture 3a: Noise Tutorial 19.

School of Electronic and Communications Engineering

DT021/4 Electronic Systems – Lecture 3a: Noise Tutorial 20.

School of Electronic and Communications Engineering

Noise Figure (cont.)


■ Consider a circuit as shown below, where S represents signal power and N represents noise power.
 ❖ N_o is the total output noise including the circuit contribution and noise transmitted from the source resistance. The noise figure is

$$F = \frac{S_i}{N_i} \cdot \frac{N_o}{S_o}$$

Noticing that $S_o = GS_i$

$$F = \frac{N_o}{G \cdot N_i}$$
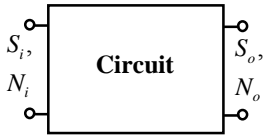
$$F = \frac{\text{Total Noise Power}}{\text{part of noise due to source resistance}}$$



DT021/4 Electronic Systems – Lecture 3a: Noise Tutorial 21.

School of Electronic and Communications Engineering

Dashed lines for student notes.

DT021/4 Electronic Systems – Lecture 3a: Noise Tutorial 22.

School of Electronic and Communications Engineering

Noise Figure (P1)

- What is meant by the *Noise Figure* of an amplifier ?
- A three-stage amplifier has an input stage which has a noise figure $F_1 = 1$ dB and a gain $G_1 = 40$ dB. The two succeeding stages have respective noise figures $F_2 = 3$ dB and $F_3 = 6$ dB and corresponding gains $G_2 = 20$ dB and $G_3 = 0$ dB.
- Determine the overall noise figure of the amplifier.
- Which stage contributes most to overall noise?

DT021/4 Electronic Systems – Lecture 3a: Noise Tutorial 23.

School of Electronic and Communications Engineering

Dashed lines for student notes.

DT021/4 Electronic Systems – Lecture 3a: Noise Tutorial 24.

Solution (P1)

$$\text{Noise Figure} \equiv \frac{\text{Total Noise Power Output}}{\text{Output Noise Due to } R_s} \equiv \frac{(S/N)_{in}}{(S/N)_{out}}$$

- The noise model for this 3-stage amplifier can be described by the following diagram

$$\text{Noise Figure} = \frac{G_1 G_2 G_3 (N_s + N_1) + G_2 G_3 N_2 + G_3 N_3}{G_1 G_2 G_3 N_s} =$$

$$= 1 + \frac{N_1}{N_s} + \frac{N_2}{G_1 N_s} + \frac{N_3}{G_1 G_2 N_s} = F_1 + \frac{F_2 - 1}{G_1} + \frac{F_3 - 1}{G_1 G_2}$$

DT021/4 Electronic Systems – Lecture 3a: Noise Tutorial 25.

Solution (P1)

$$\text{Noise Figure} \equiv \frac{\text{Total Noise Power Output}}{\text{Output Noise Due to } R_s} \equiv \frac{(S/N)_{in}}{(S/N)_{out}}$$

$$\text{Noise Figure} = \frac{G_1 G_2 G_3 (N_s + N_1) + G_2 G_3 N_2 + G_3 N_3}{G_1 G_2 G_3 N_s} =$$

$$= 1 + \frac{N_1}{N_s} + \frac{N_2}{G_1 N_s} + \frac{N_3}{G_1 G_2 N_s} = F_1 + \frac{F_2 - 1}{G_1} + \frac{F_3 - 1}{G_1 G_2}$$

DT021/4 Electronic Systems – Lecture 3a: Noise Tutorial 26.

Solution (P1)

- $F_1 = 1 \text{ dB} \equiv 1.259$
- $F_2 = 3 \text{ dB} \equiv 1.99$
- $F_3 = 6 \text{ dB} \equiv 3.98$
- $G_1 = 40 \text{ dB} \equiv 100$
- $G_2 = 20 \text{ dB} \equiv 10$
- $G_3 = 0 \text{ dB} \equiv 1$

$$F = 1 + (F_1 - 1) + (F_2 - 1)/G_1 + (F_3 - 1)/G_1 G_2$$

$$F = 1.259 + (1.995 - 1)/100 + (3.98 - 1)/(100 \times 10) =$$

$$= 1.259 + 0.995/100 + 2.98/1000 =$$

$$= 1 + 0.259 + 0.00995 + 0.00298 = 1.272 \equiv 1.044 \text{ dB}$$

- Contributions

DT021/4 Electronic Systems – Lecture 3a: Noise Tutorial 27.

Solution (P1)

$$\text{Noise Figure} \equiv \frac{\text{Total Noise Power Output}}{\text{Output Noise Due to } R_s} \equiv \frac{(S/N)_{in}}{(S/N)_{out}}$$

$$\text{Noise Figure} = \frac{G_1 G_2 G_3 (N_s + N_1) + G_2 G_3 N_2 + G_3 N_3}{G_1 G_2 G_3 N_s} =$$

$$= 1 + \frac{N_1}{N_s} + \frac{N_2}{G_1 N_s} + \frac{N_3}{G_1 G_2 N_s} = F_1 + \frac{F_2 - 1}{G_1} + \frac{F_3 - 1}{G_1 G_2}$$

DT021/4 Electronic Systems – Lecture 3a: Noise Tutorial 28.

Equivalent input noise Generators

- The **equivalent input noise** voltage for a particular configuration is dependent on the source resistance R_S , as well as the transistor parameters.
- This method is now extended to a more general and more useful representation by using **two** equivalent input noise generators:
 - equivalent input **voltage**
 - equivalent input **current**

DT021/4 Electronic Systems – Lecture 3a: Noise Tutorial 29.

School of Electronic and Communications Engineering

D.T.T.

DT021/4 Electronic Systems – Lecture 3a: Noise Tutorial 30.

Noise Figure vs. R_S

- For very **low** values of R_S , the **v**-generator is dominant, whereas for **large** R_S the **i**-generator is the most important.
- It is apparent, that **F** has a minimum as R_S varies.
- By differentiating **F** with respect to R_S , we can calculate the value of R_S giving minimum **F**:

$$R_{S\ opt}^2 = \overline{v_{IN}^2} / \overline{i_{IN}^2}$$

DT021/4 Electronic Systems – Lecture 3a: Noise Tutorial 31.

School of Electronic and Communications Engineering


D.T.T.

DT021/4 Electronic Systems – Lecture 3a: Noise Tutorial 32.

Noise model for 741

- Noise model for OpAmp circuits is presented below,
- The concrete form for input noise generators depends on particular circuit design

For 741 OpAmp these expressions are:

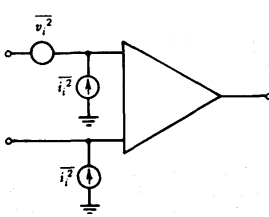

$$\frac{\overline{v_i^2}}{B} = 4kT(16000)$$

$$\frac{\overline{i_i^2}}{B} = 2qI_B \approx 2q(0.2 \cdot 10^{-6})$$

DT021/4 Electronic Systems – Lecture 3a: Noise Tutorial 33.


School of Electronic and Communications Engineering

D.T.T.

DT021/4 Electronic Systems – Lecture 3a: Noise Tutorial 34.

(P2) OpAmp Noise

- The amplifier circuit shown in Fig. 1 has an effective noise bandwidth of 5 MHz. Given that the differential amplifier has equivalent input noise current and voltage densities of 1 pA/ $\sqrt{\text{Hz}}$ and 1 nV/ $\sqrt{\text{Hz}}$ respectively
- sketch the noise equivalent circuit and hence determine values for:
 - (a) The equivalent input noise current and voltage of the circuit (excluding the source);
 - (b) The output signal-to-noise (S/N) ratio, given a 1 V (rms) sinusoidal source (V_s) and a 10 k Ω source resistance (R_s);
 - (c) The noise figure (F) of the amplifier circuit.
- Assume that $4kT = 1.65 \times 10^{-20}$ J.

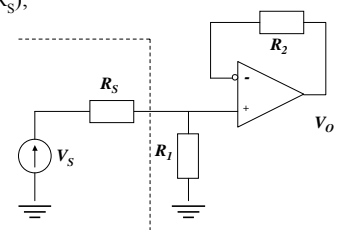

DT021/4 Electronic Systems – Lecture 3a: Noise Tutorial 35.

School of Electronic and Communications Engineering

D.T.T.

DT021/4 Electronic Systems – Lecture 3a: Noise Tutorial 36.

Solution (P2a)

- The noise equivalent circuit consists of two equivalent input noise currents i_i and one voltage v_i and
- two thermal noises (spectral densities) from R_1 and R_2 - i_1 and i_2

$$\overline{i_1^2} = 4kT / R_1 = 1.65 \times 10^{-25} \text{ A}^2/\text{Hz}$$

$$\overline{i_2^2} = 4kT / R_2 = 1.65 \times 10^{-24} \text{ A}^2/\text{Hz}$$

$$\overline{i_1^2} = 10^{-24} \text{ A}^2 / \text{Hz}$$

$$\overline{v_i^2} = 10^{-18} \text{ V}^2 / \text{Hz}$$

DT021/4 Electronic Systems – Lecture 3a: Noise Tutorial 37.

DT021/4 Electronic Systems – Lecture 3a: Noise Tutorial 38.

Solution (P2a)

For open-circuit inputs:

The output of the circuit in Fig.2 is
$$\overline{v_o^2} = (\overline{i_1^2} + \overline{i_i^2})R_1^2 + \overline{v_i^2} + (\overline{i_2^2} + \overline{i_i^2})R_2^2 \quad (1)$$

The output of the circuit in Fig.3 is
$$\overline{v_o^2} = \overline{i_n^2}R_1^2 \quad (2)$$

Equating (1) and (2) gives the expression for the equivalent input noise current

$$\overline{i_n^2} = (\overline{i_1^2} + \overline{i_i^2}) + \overline{v_i^2} / R_1^2 + (\overline{i_2^2} + \overline{i_i^2})R_2^2 / R_1^2$$

DT021/4 Electronic Systems – Lecture 3a: Noise Tutorial 39.

DT021/4 Electronic Systems – Lecture 3a: Noise Tutorial 40.

Solution (P2a)

Hence

$$\begin{aligned} \overline{i_n^2} &= (\overline{i_1^2} + \overline{i_i^2}) + \overline{v_i^2} / R_1^2 + (\overline{i_i^2} + \overline{i_2^2}) R_2^2 / R_1^2 = \\ &= (10^{-24} + 0.165 \cdot 10^{-24}) + 10^{-18} / 10^{10} + (10^{-24} + 1.65 \cdot 10^{-24}) / 10^2 \\ &= 1.165 \cdot 10^{-24} + 10^{-28} + 1.165 \cdot 10^{-26} = 1.182 \cdot 10^{-24} \text{ A}^2 / \text{Hz} \end{aligned}$$

$$i_n = \sqrt{\overline{i_n^2} \times \Delta f} = \sqrt{1.182 \cdot 10^{-24} \times 5 \cdot 10^6} = 2.43 \text{ nA}$$

DT021/4 Electronic Systems – Lecture 3a: Noise Tutorial 41.

School of Electronic and Communications Engineering

DIT

DT021/4 Electronic Systems – Lecture 3a: Noise Tutorial 42.

Solution (P2a)

For short-circuit inputs:

The output of the circuit in Fig.2 is $\overline{v_o^2} = \overline{v_i^2} + (\overline{i_1^2} + \overline{i_2^2}) R_2^2$ (3)

The output of the circuit in Fig.3 is $\overline{v_o^2} = \overline{v_n^2}$ (4)

Equating (3) and (4) gives the expression for the equivalent input noise voltage

$$\overline{v_n^2} = \overline{v_i^2} + (\overline{i_1^2} + \overline{i_2^2}) R_2^2 = 10^{-18} + (10^{-24} + 1.65 \cdot 10^{-24}) \times 10^8 \approx 2.65 \cdot 10^{-16} \text{ V}^2 / \text{Hz}$$

$$v_n = \sqrt{\overline{v_n^2} \times \Delta f} = \sqrt{2.65 \cdot 10^{-16} \times 5 \cdot 10^6} = 35.8 \text{ } \mu\text{V}$$

DT021/4 Electronic Systems – Lecture 3a: Noise Tutorial 43.

School of Electronic and Communications Engineering

DIT

DT021/4 Electronic Systems – Lecture 3a: Noise Tutorial 44.

Solution (P2b)

(b) determine the output S/N, $V_S = 1 \text{ V (rms)}$ and $R_S = 10 \text{ k}\Omega$

$$\overline{v_{on}^2} = \frac{(\overline{i_n^2} + \overline{i_s^2})(R_1 \times R_S)^2}{(R_1 + R_S)^2} + \frac{\overline{v_n^2} R_1^2}{(R_1 + R_S)^2} =$$

$$= \frac{(1.182 \cdot 10^{-24} + 4kT/10k\Omega)(100k\Omega \times 10k\Omega)^2}{(100k\Omega + 10k\Omega)^2} + \frac{2.575 \cdot 10^{-16} \times (100k\Omega)^2}{(100k\Omega + 10k\Omega)^2} =$$

$$= \frac{(1.182 \cdot 10^{-24} + 1.65 \cdot 10^{-24})(10^9 \Omega)^2}{(1.1 \cdot 10^5 \Omega)^2} + 2.13 \cdot 10^{-16} =$$

$$= 2.35 \cdot 10^{-16} + 2.13 \cdot 10^{-16} = 4.475 \cdot 10^{-16} \text{ V}^2 / \text{Hz}$$

DT021/4 Electronic Systems – Lecture 3a: Noise Tutorial 45.

DT021/4 Electronic Systems – Lecture 3a: Noise Tutorial 46.

Solution (P2b,c)

$$v_{on} = \sqrt{\overline{v_{on}^2} \times \Delta f} = \sqrt{4.475 \cdot 10^{-16} \times 5 \cdot 10^6} = 47 \mu\text{V}$$

$$V_{oS} = \frac{R_1}{R_1 + R_S} \times 1\text{V} = \frac{100k\Omega}{100k\Omega + 10k\Omega} \times 1\text{V} \approx 0.9\text{V}$$

$$S/N_{out} = 0.9 \text{ V} / 47 \mu\text{V} = 19148 \approx 85.64 \text{ dB}$$

(c) (determine) The noise figure (F) of the amplifier circuit

$$F \equiv \frac{S/N_{in}}{S/N_{out}}$$

$$S/N_{in} = \frac{v_s}{v_{sn}} = \frac{v_s}{\sqrt{4kT/R_S \times \Delta f}} = 35749 \approx 91 \text{ dB}$$

$$F = \frac{S/N_{in}}{S/N_{out}} = \frac{35749}{19148} = 1.84$$

$$F(\text{dB}) = 10 \log(F) = 10 \log(1.84) = 2.66 \text{ dB}$$

DT021/4 Electronic Systems – Lecture 3a: Noise Tutorial 47.

DT021/4 Electronic Systems – Lecture 3a: Noise Tutorial 48.

Solution (P2 additional)

(d) Determine the optimal value of R_s for amplifier circuit

Solution: the optimal value of R_s is

$$R_{Sopt} = v_n / i_n = 35 \mu V / 2.43 nA = 14.7 k\Omega$$

(e) Determine the noise figure (F) of the circuit with optimal R_s

Solution: Repeat (c)-(d)

$$F_{opt} = 1.79 \quad F_{opt} (dB) = 2.54 dB$$

DT021/4 Electronic Systems – Lecture 3a: Noise Tutorial 49.

School of Electronics and Communications Engineering

D.T.T.

DT021/4 Electronic Systems – Lecture 3a: Noise Tutorial 50.

(P3) BJT Noise

- The transistor used in the common-emitter circuit shown in Fig.3 has an equivalent input noise spectral density values of $1 \text{ nV}/\sqrt{\text{Hz}}$ and $1 \text{ pA}/\sqrt{\text{Hz}}$ and device a.c. parameter values $g_m = 100 \text{ mA/V}$ and $r_{be} = 1 \text{ k}\Omega$. The load resistance value $R = 10 \text{ k}\Omega$. Bias circuitry has been omitted. Determine:
- (i) The equivalent input noise voltage and current spectral densities at the amplifier input (X).
- (ii) The optimum value of source resistance R_s which should be used.

DT021/4 Electronic Systems – Lecture 3a: Noise Tutorial 51.

School of Electronics and Communications Engineering

D.T.T.

DT021/4 Electronic Systems – Lecture 3a: Noise Tutorial 52.

Solution (P3a)

▪ For open circuit inputs $i_o^2 = g_m^2 r_{be}^2 i_n^2 + i_r^2 = g_m^2 r_{be}^2 i^2$

$$i^2 = i_n^2 + \frac{i_r^2}{g_m^2 r_{be}^2} = (1 \text{ pA} / \sqrt{\text{Hz}})^2 + \frac{4kT / R}{g_m^2 r_{be}^2} =$$

$$= 10^{-24} \text{ A}^2 / \text{Hz} + \frac{4 \times 1.38 \times 10^{-23} \text{ J/K} \cdot 298 \text{ K} / 10^4 \Omega}{(0.1 \text{ A/V} \times 1000 \Omega)^2} =$$

$$= 10^{-24} \text{ A}^2 / \text{Hz} + \frac{1.65 \times 10^{-24} \text{ A}^2 / \text{Hz}}{10^4} =$$

$$10^{-24} \text{ A}^2 / \text{Hz} + 1.65 \times 10^{-28} \text{ A}^2 / \text{Hz} \approx 10^{-24} \text{ A}^2 / \text{Hz}$$

DT021/4 Electronic Systems – Lecture 3a: Noise Tutorial 53.

DT021/4 Electronic Systems – Lecture 3a: Noise Tutorial 54.

Solution (P3a,b)

▪ For short circuit inputs $i_o^2 = g_m^2 v_n^2 + i_r^2 = g_m^2 v^2$

$$v^2 = v_n^2 + i_r^2 / g_m^2 = 10^{-18} \text{ V}^2 / \text{Hz} + \frac{1.65 \cdot 10^{-24} \text{ A}^2 / \text{Hz}}{10^{-2} \text{ A}^2 / \text{V}^2} =$$

$$= 10^{-18} \text{ V}^2 / \text{Hz} + 1.65 \cdot 10^{-22} \text{ V}^2 / \text{Hz} = 1.000165 \cdot 10^{-18} \text{ V}^2 / \text{Hz}$$

(b) The optimum R_s is

$$R_s = \sqrt{v^2 / i^2} = \sqrt{10^{-18} \text{ V}^2 / \sqrt{\text{Hz}} / 10^{-24} \text{ A}^2 / \sqrt{\text{Hz}}} = \sqrt{10^6 \Omega^2} = 1 \text{ k}\Omega$$

DT021/4 Electronic Systems – Lecture 3a: Noise Tutorial 55.

DT021/4 Electronic Systems – Lecture 3a: Noise Tutorial 56.

Problem 4

- The voltage source of 100mV with resistance 1 kΩ is connected to the amplifier with 10 kΩ input resistance and 20 dB gain. The amplifier has an equivalent input noise spectral density values of 1 μV/√Hz and 1 nA/√Hz. The load resistance value R = 100 kΩ and frequency bandwidth B = 1 MHz. Determine:
 - (a) The noise figure (F)
 - (b) The output signal-to-noise (S/N) ratio;
 - (c) The optimum value of source resistance R_s .
 - (d) The optimised noise figure and output signal-to-noise ratio.
- Assume that $4kT = 1.656 \times 10^{20}$ J

DT021/4 Electronic Systems – Lecture 3a: Noise Tutorial 57.

DT021/4 Electronic Systems – Lecture 3a: Noise Tutorial 58.

P4 Solution (cont.)

- Consider the circuit below, consisting of the noise generators and signal source

- ❖ The noise at input terminals from the noise generators is

$$v_{xA} = v_i \frac{z_i}{z_i + R_s} + i_i \frac{z_i R_s}{z_i + R_s}$$

and thus


$$\overline{v_{xA}^2} = \overline{v_i^2} \frac{|z_i|^2}{|z_i + R_s|^2} + \overline{i_i^2} \frac{|z_i R_s|^2}{|z_i + R_s|^2}$$

DT021/4 Electronic Systems – Lecture 3a: Noise Tutorial 59.

DT021/4 Electronic Systems – Lecture 3a: Noise Tutorial 60.

(P5) EF BJT Noise

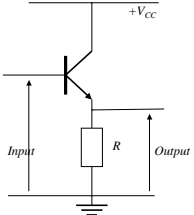
- The BJT device contained in the circuit shown in Fig. 1 has an equivalent input noise voltage of $e_n = 1 \text{ nV}/\sqrt{\text{Hz}}$ and an equivalent input noise current of $i_n = 1 \text{ pA}/\sqrt{\text{Hz}}$ at a particular spot frequency. Given the following relevant transistor parameter and resistor values:
 - $r_{be} = 1 \text{ k}\Omega$; $g_m = 0.1 \text{ A/V}$; $R = 1 \text{ k}\Omega$



- determine the corresponding equivalent input noise voltage and current values (I/Hz) for the circuit and the optimum value of source resistance required. Assume that $4kT = 1.656 \times 10^{-20}$.

(P5) EF BJT Noise

(P5) EF BJT Noise

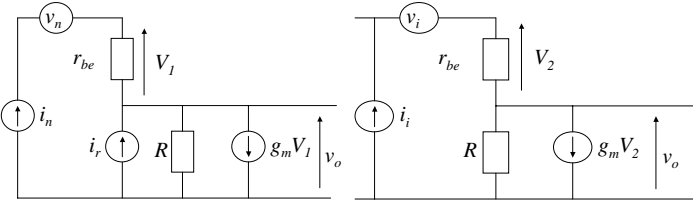

- For short circuit inputs: $\bar{V}_o = R[\bar{i}_r + \bar{V}_1(g_m + 1/r_{be})] = \bar{i}_r R + \frac{R(g_m + 1/r_{be})(\bar{v}_n + \bar{i}_n R)}{1 + Rg_m + R/r_{be}}$

$$\bar{V}_1 = \frac{\bar{v}_n + \bar{i}_n R}{1 + g_m R + R/r_{be}} \quad \bar{V}_o = R[g_m + 1/r_{be}]\bar{V}_2 = \frac{R[g_m + 1/r_{be}]\bar{V}_1}{1 + R[g_m + 1/r_{be}]}$$

$$\bar{V}_i = \bar{V}_2 + R[g_m + 1/r_{be}]\bar{V}_2 \quad \bar{V}_2 = \frac{\bar{V}_i}{1 + R[g_m + 1/r_{be}]}$$

$$\bar{v}_n = \bar{V}_1 + R[\bar{i}_r + g_m \bar{V}_1 + \bar{V}_1/r_{be}] = \bar{V}_1 + R[\bar{i}_r + \bar{V}_1(g_m + 1/r_{be})]$$

(P5) EF BJT Noise

(P6) CB BJT Noise

- A common-base amplifier with a load resistance of 1 kΩ and operating at a quiescent (collector) current of 2.5 mA has parameter values of $g_m = 100 \text{ mA/V}$ and $r_{be} = 2 \text{ k}\Omega$.
- It is suggested that a reduction in quiescent current would allow the input impedance of the amplifier to match that of a 500 signal source. To what value should the quiescent current be lowered?
- Solution**

Input impedance $Z_{in} = \frac{r_{be}}{1 + g_m r_{be}} \approx \frac{1}{g_m}$

- At $I_C = 2.5 \text{ mA}$, $g_m = 0.1 \text{ A/V}$, $Z_{in} = 10 \Omega$
- At $I_C = 0.5 \text{ mA}$, $g_m = 0.02 \text{ A/V}$, $Z_{in} = 50 \Omega$

DT021/4 Electronic Systems – Lecture 3a: Noise Tutorial 73.

(P6) CB BJT Noise

- Determine the (mid-band) power spectral density of the noise observed at the output of the amplifier in the case of the revised quiescent current value given that the transistor has equivalent input current and voltage noise source values of $1 \text{ pA}/\sqrt{\text{Hz}}$ and $1 \text{ nV}/\sqrt{\text{Hz}}$ respectively.
- Is the reduction in quiescent current likely to improve or disimprove noise performance?
- Assume that $4kT = 1.656 \times 10^{20} \text{ J}$.

DT021/4 Electronic Systems – Lecture 3a: Noise Tutorial 74.

(P6) CB BJT Noise

$$V^2 = \left[\frac{V_n^2 + V_s^2}{R_s^2} + i_n^2 \right] \left[\frac{r_{be} R_s}{r_{be} + R_s} \right]^2$$

$$V_o^2 = (g_m^2 V^2 + i_R^2) R^2$$

$$V_o^2 = \left(\left[\frac{V_n^2 + V_s^2}{R_s^2} + i_n^2 \right] \left[\frac{r_{be} R_s g_m}{r_{be} + R_s} \right]^2 + i_R^2 \right) R^2$$

$g_m = 0.02$; $r_{be} = 10 \text{ k}\Omega$; $R_s = 50 \Omega$; $V_n^2 = (1 \text{ nV})^2$; $i_n^2 = (1 \text{ pA})^2$;
 $V_s^2 = 4kTR_s$; $i_R^2 = 4kT / R_s$; $g_m r_{be} = 200$;

$$V_o^2 = \left(\left[\frac{10^{-18} + 1.656 \cdot 10^{-20} \times 50}{2500} + 10^{-24} \right] \left[\frac{200 \times 50}{10 \text{ k}\Omega + 50 \Omega} \right]^2 + 1.656 \cdot 10^{-20} / 50 \right) \cdot 10^6 =$$

$$= \left(\left[\frac{10^{-18} + 0.828 \cdot 10^{-18}}{2500} + 10^{-24} \right] \times 0.99 + 3.31 \cdot 10^{-18} \right) \cdot 10^6 =$$

$$= (7.322 \cdot 10^{-22} \times 0.99 + 1.656 \cdot 10^{-23}) \cdot 10^6 \approx 7.41 \cdot 10^{-16} \text{ V}^2 / \text{Hz}$$

DT021/4 Electronic Systems – Lecture 3a: Noise Tutorial 75.

(P6) CB BJT Noise

- $v_o = 27.23 \text{ nV}/\sqrt{\text{Hz}}$,
- Note if $g_m \downarrow$, then $r_{be} \uparrow$
- Reduction in quiescent current will increase r_{be} , i.e. the noise performance should be improved

$$V_o^2 = \left(\left[\frac{V_n^2 + V_s^2}{R_s^2} + i_n^2 \right] \left[\frac{r_{be} R_s g_m}{r_{be} + R_s} \right]^2 + i_R^2 \right) R^2$$

DT021/4 Electronic Systems – Lecture 3a: Noise Tutorial 76.