

Electronic Noise

- Dynamic range in the analog domain
 - Resistor noise
 - Amplifier noise
 - Maximum signal levels
- Tow-Thomas Biquad noise example
- Implications on power dissipation

Analog Dynamic Range

- Finite precision effects in digital filters are rapidly becoming negligible
 - Floating point digital filters with huge mantissas will be reduced to negligible cost
 - The only fixed-point numbers will come from ADCs
- But we will always have thermal noise

Analog Dynamic Range

- Let's say you've selected the poles and zeroes of your analog filter transfer function
- Of the infinitely many ways to build a filter with a given transfer function, **each of those ways has a different output noise!**

Analog Dynamic Range


- The job of a high-performance analog filter designer is to get reasonably close to the optimal noise for a given transfer function
 - Not the absolute minimum noise, just close
- The job of a mixed-signal chip architect is to appreciate filter noise and to be able to model filters well enough to know that a given dynamic range objective is feasible

Analog Dynamic Range

- We'll begin our adventure in analog filter implementation by looking at the noise in resistors and simple RC filters...

Resistor Noise

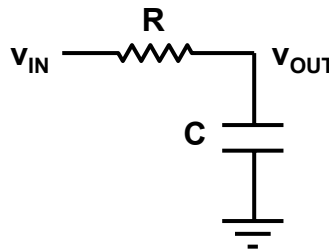- Capacitors are noiseless
- Resistors have thermal noise
 - This noise is uniformly distributed from dc to infinity
 - Frequency-independent noise is called “white noise”




Resistor Noise

- Resistor noise has
 - A mean value of zero
 - A mean-squared value

$$\overline{v_n^2} = 4k_B T_r R \Delta f$$

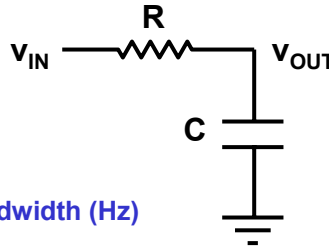Volts² (pointing to $\overline{v_n^2}$)
 ohms (pointing to R)
 absolute temperature (°K) (pointing to T_r)
 measurement bandwidth (Hz) (pointing to Δf)




Boltzmann's constant = 1.38e-23 J/°K

Resistor Noise


- Resistor rms noise voltage in a 10Hz band centered at 1kHz is the same as resistor rms noise in a 10Hz band centered at 1GHz
- Resistor noise spectral density, N_0 , is the rms noise per $\sqrt{\text{Hz}}$ of bandwidth:
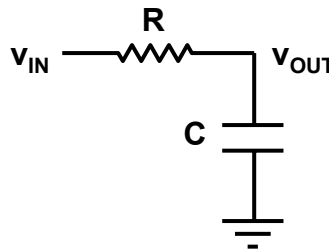
$$N_0 = \sqrt{\frac{\overline{v_n^2}}{\Delta f}} = \sqrt{4k_B T_r R}$$




Resistor Noise

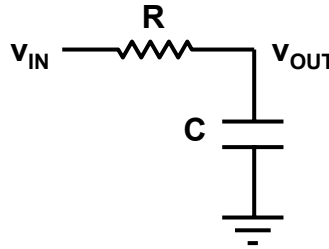- Don't bother to remember Boltzmann's constant
- Instead, remember forever that N_0 for a **1k Ω** resistor at room temperature is **4nV/ $\sqrt{\text{Hz}}$**
- Scaling R,
 - A 10M Ω resistor gives 400nV/ $\sqrt{\text{Hz}}$
 - A 50 Ω resistor gives 0.9nV/ $\sqrt{\text{Hz}}$
- Or, remember that $k_B T_r = 4 \times 10^{-21} \text{ J}$ ($T_r = 17 \text{ }^\circ\text{C}$)



Resistor Noise

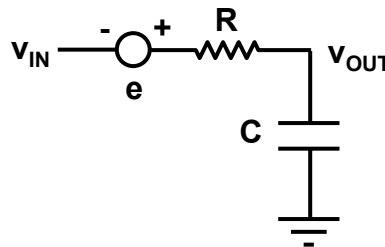- Resistor noise gives our filter a non-zero output when $v_{IN}=0$
- In this simple example, both the input signal and the resistor noise obviously have the same transfer functions to the output
- Since noise has random phase, we can use any polarity convention for a noise source (but we have to use it consistently)




Resistor Noise


- What is the thermal noise of the RC filter?
- Let's ask SPICE!
Netlist:

```

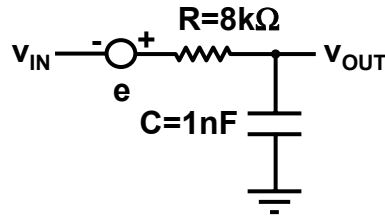Noise from RC LPF
vin vin 0 ac 1V
r1 vin vout 8kOhm
c1 vout 0 1nF
.ac dec 100 10Hz 1GHz
.noise V(vout) vin
.end
    
```



LPF1 Output Noise Density

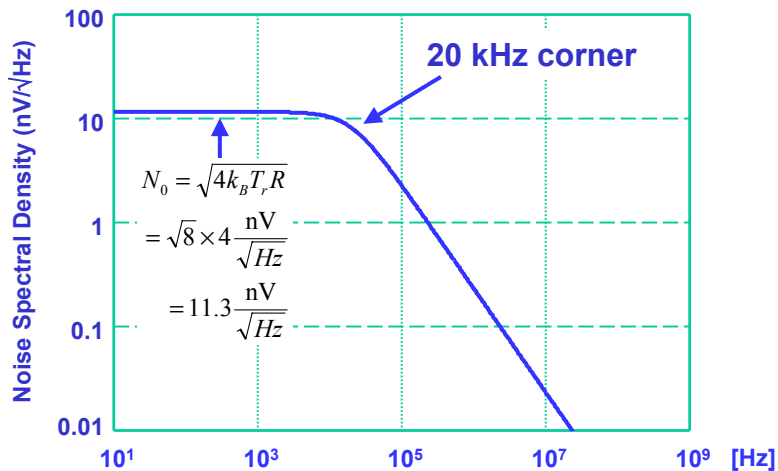

Total Noise

- Suppose we want to know the value of v_o “now”, what’s the standard deviation error? (E.g. on the display of a volt-meter connected to v_o).

- Answer:

$$\overline{v_o^2} = \int_0^{\infty} 4k_B TR |H(2\pi jf)|^2 df$$

Total Noise

- Note that noise is integrated in the mean-squared domain, because noise in a bandwidth df around frequency f_1 is uncorrelated with noise in a bandwidth df around frequency f_2
 - Powers of uncorrelated random variables add
 - Squared transfer functions appear in the mean-squared integral

Total Noise

$$\begin{aligned}\overline{v_o^2} &= \int_0^{\infty} 4k_B TR |H(2\pi jf)|^2 df \\ &= \int_0^{\infty} 4k_B TR \left| \frac{1}{1 + 2\pi jfRC} \right|^2 df \\ &= \frac{k_B T}{C}\end{aligned}$$

Total Noise


$$\overline{v_o^2} = \frac{k_B T}{C}$$

- This interesting and somewhat counterintuitive result means that even though resistors provide the noise sources, capacitors set the total noise
- For a given capacitance, as resistance goes up, the increase in noise density is balanced by a decrease in noise bandwidth

kT/C Noise

- The rms noise voltage of the simplest possible (first order) filter is $\sqrt{k_B T/C}$
- For 1pF, $\sqrt{k_B T/C} = 64 \mu\text{V-rms}$ (at 298°K)
- 1000pF gives 2 $\mu\text{V-rms}$
- The noise of a more complex filter is $\sqrt{K \times k_B T/C}$
K depends on implementation and features such as filter order


LPF1 Output Noise

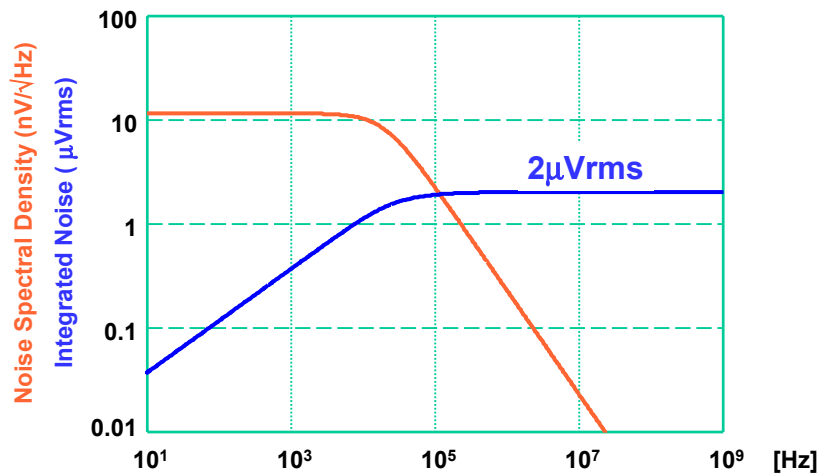

LPF1 Output Noise

- Note that the integrated noise essentially stops growing above 100kHz for this 20kHz lowpass filter
- Beware of faulty intuition which might tempt you to believe that an 80Ω , 1000pF filter has lower integrated noise than our 8000Ω , 1000pF filter...


LPF1 Output Noise

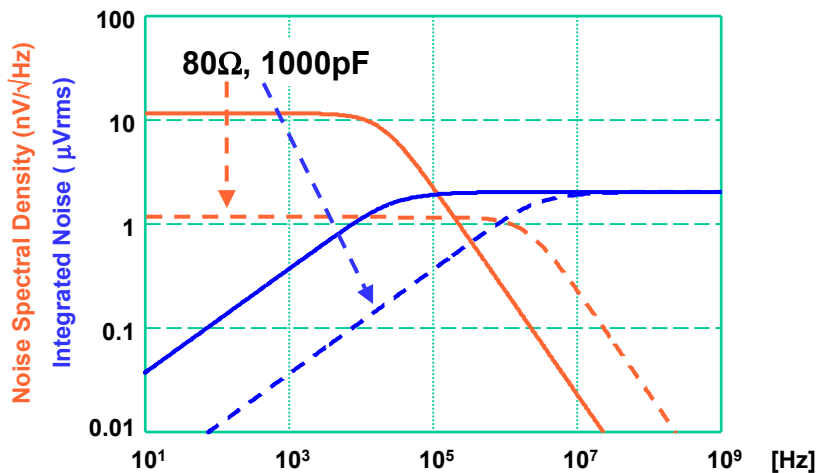

LPF1 Output Noise

- Of course, an 80Ω , $100,000\text{pF}$ filter has both the same bandwidth AND lower integrated noise than our 8000Ω , 1000pF filter
- In the analog filter dynamic range game, the highest capacitance wins

LPF1 Output Noise

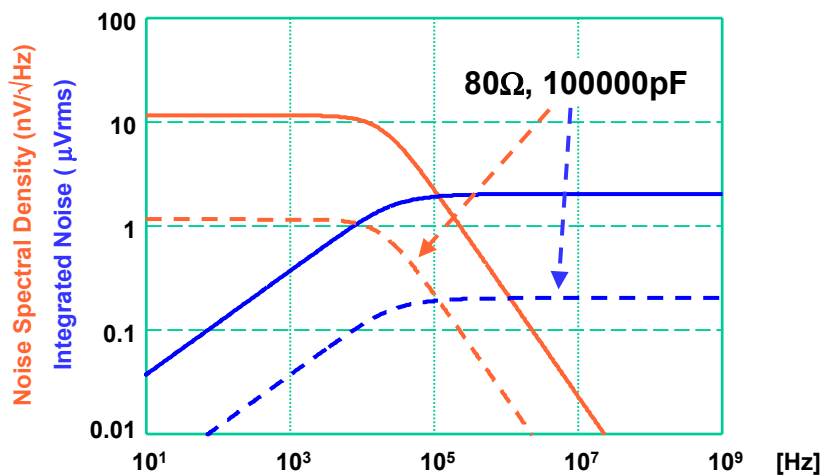

Analog Circuit Dynamic Range

- The biggest signal we can ever expect at the output of a circuit is limited by the supply voltage, V_{DD} hence (for sinusoids)

$$V_{\max}(rms) = \frac{1}{\sqrt{2}} \frac{V_{DD}}{2}$$

- The noise is

$$V_n(rms) = \sqrt{K \frac{k_B T}{C}}$$

- So the dynamic range in dB is:

$$\begin{aligned} DR &= \frac{V_{\max}(rms)}{V_n(rms)} = \frac{V_{DD} \sqrt{C}}{\sqrt{8Kk_B T}} \quad [V/V] \\ &= 20 \log_{10} \left(V_{DD} \sqrt{\frac{C}{K}} \right) + 75 \quad [\text{dB}] \quad \text{with } C \text{ in [pF]} \end{aligned}$$

Analog Circuit Dynamic Range

- For integrated circuits built in modern CMOS processes, $V_{DD} < 3V$ and $C < 1nF$ ($K = 1$)
 - DR < 110dB
- For PC board circuits built with “old-fashioned” 30V opamps and discrete capacitors of < 100nF
 - DR < 140dB
 - A 30dB advantage!

Dynamic Range versus Bits

- Bits and dB are related:

$$DR = 2 + 6N \quad [\text{dB}]$$

– see “quantization noise”, later in the course

- Hence

110 dB → 18 Bits

140 dB → 23 Bits

Dynamic Range versus Power

- Each extra bit corresponds to 6dB
- 6dB means cutting noise power by 4!
- This translates into 4x larger capacitors
- To drive these at the same speed, G_m must increase 4x
- Power is proportional to G_m (for fixed supply and V_{dsat})

In analog circuits that are limited by thermal noise,

1 extra bit costs 4x power

E.g. 16Bit ADC at 200mW → 17Bit ADC at 800mW

Do not overdesign the dynamic range of analog circuits!

P.S. What is the cost of an extra bit in a 64Bit adder?

Active Filter Example


Frequency response:

$$H(s) = -\frac{1}{1 + sRC}$$

Total noise (see EE240):


$$\sqrt{V_o^2} = \sqrt{2 \frac{k_B T}{C}}$$

$$K = 2$$

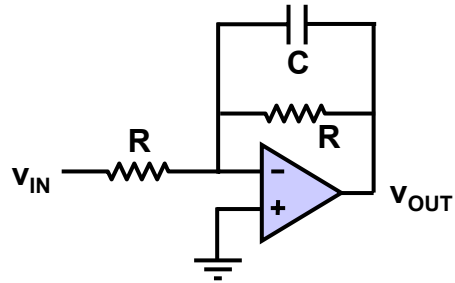

- Noise depends on filter topology
- Opamps contribute yet more noise ...

Behavioral Opamp Model

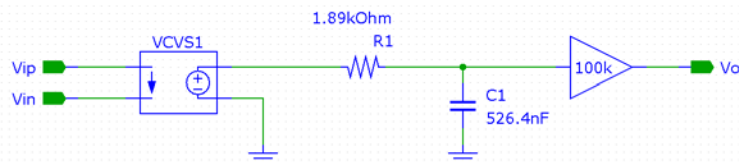

Specification


Gain G
 Unity-gain bandwidth f_u
 Input ref'd thermal noise

Example

100k
 100 MHz
 5 nV/ $\sqrt{\text{Hz}}$


Beware of flicker noise and input current noise (BJTs).

SPICE Analysis

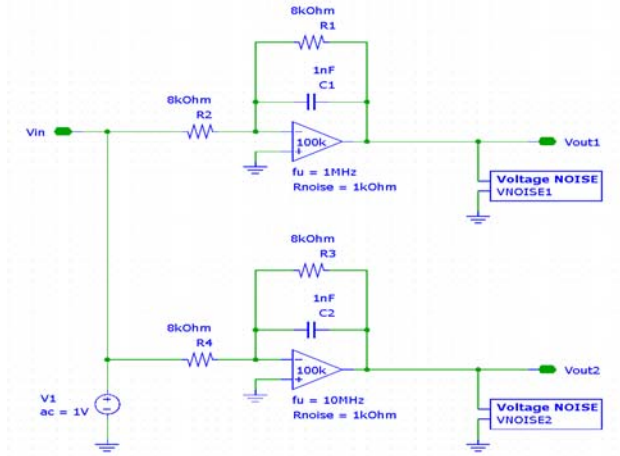

Noise Analysis

Opamp noise dominates in this example

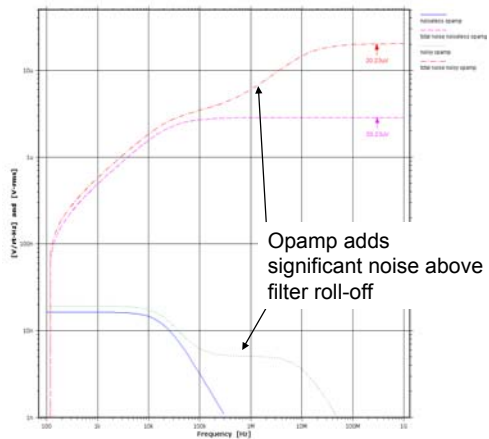


Opamp Bandwidth


Minimize opamp bandwidth:

- $f_u = 1\text{MHz} \rightarrow 7\mu\text{V-rms}$
- $f_u = 10\text{MHz} \rightarrow 20\mu\text{V-rms}$

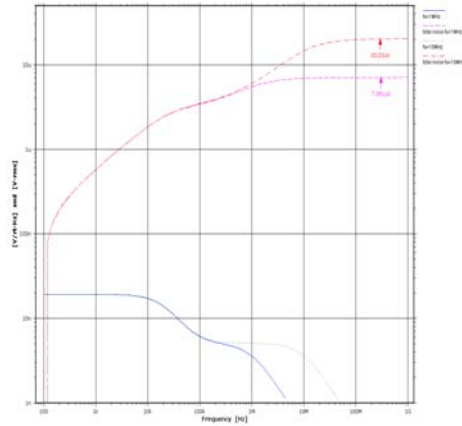Of course, the opamp has to be fast enough to faithfully realize the 20kHz corner!



Frequency Response

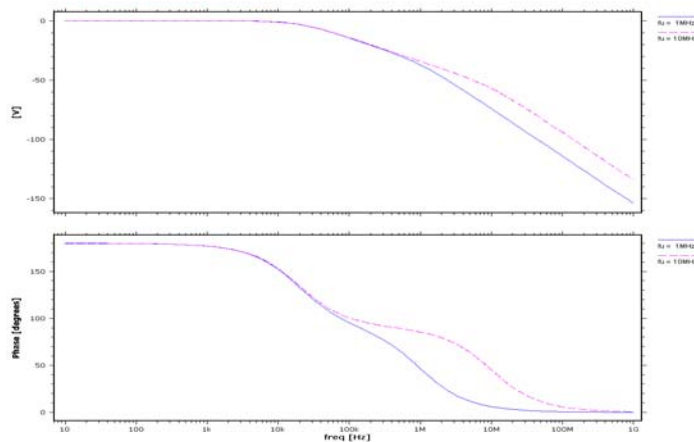


Tow-Thomas Noise Analysis

Tow-Thomas Noise Analysis

AC Analysis AC1
log sweep from 10 to 1G (501 steps)

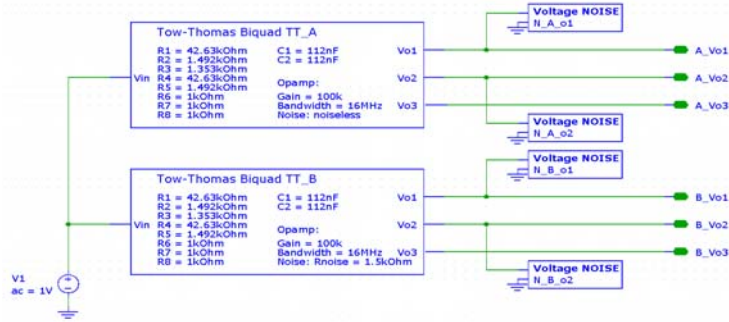AC Analysis AC2
sweep from 900 to 1.1k (201 steps)




Tow-Thomas Biquad


Tow-Thomas Biquad

K = 1 (multiplies C, divides R)

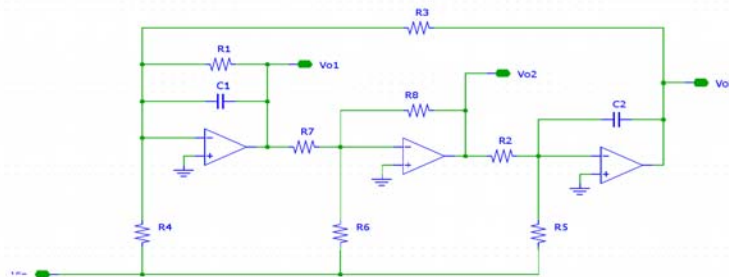C1 = 112nF, R1 = 42.63kOhm, R3 = 1.353kOhm, R5 = 1.492kOhm, R7 = 1kOhm
 C2 = 112nF, R2 = 1.492kOhm, R4 = 42.63kOhm, R6 = 1kOhm, R8 = 1kOhm
 OpAmp Bandwidth = 16MHz, Noise: Rnoise = 1.5kOhm




Bandpass Noise

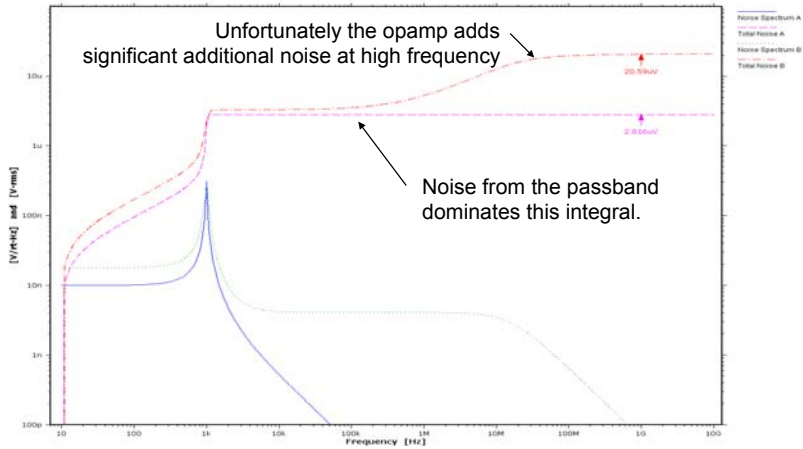


RC Filter Reduces BP Noise

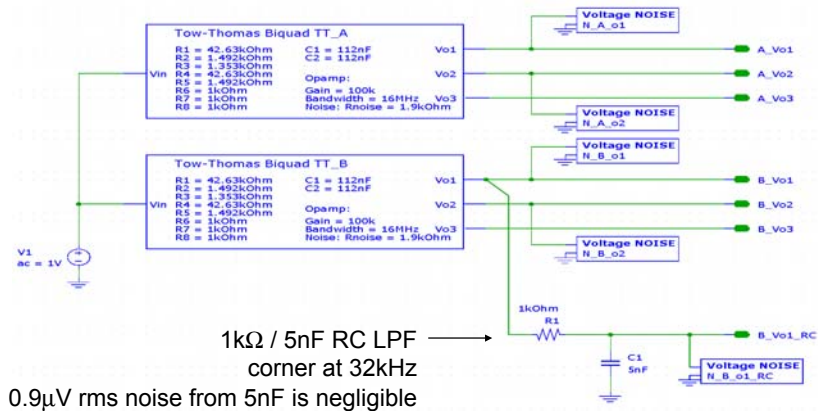
We cannot reduce the opamp noise or bandwidth ... let's filter its noise!



BP Response with RC Filter

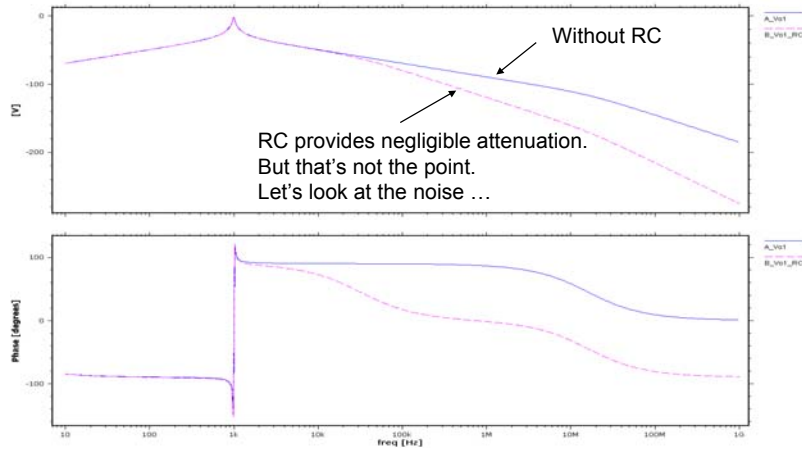


BP Noise after RC Filter

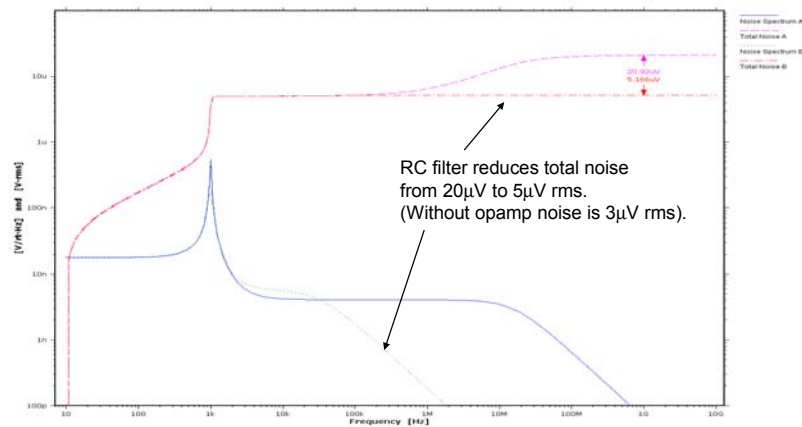


BP Dynamic Range

- Maximum sinewave input: 7.8V rms (limited by opamp)
 - Noise: 5.2 μ V rms (with RC)
 - Dynamic range: **123dB**
- No IC with integrated capacitors can get close to this dynamic range


Bandstop Noise

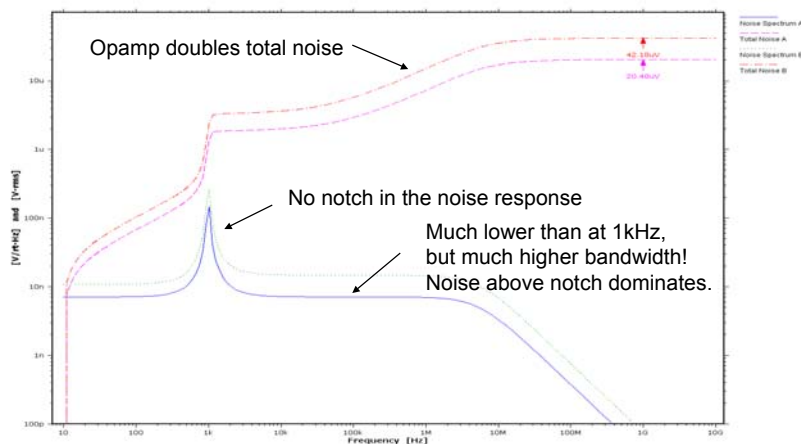

Noise versus Pole Q

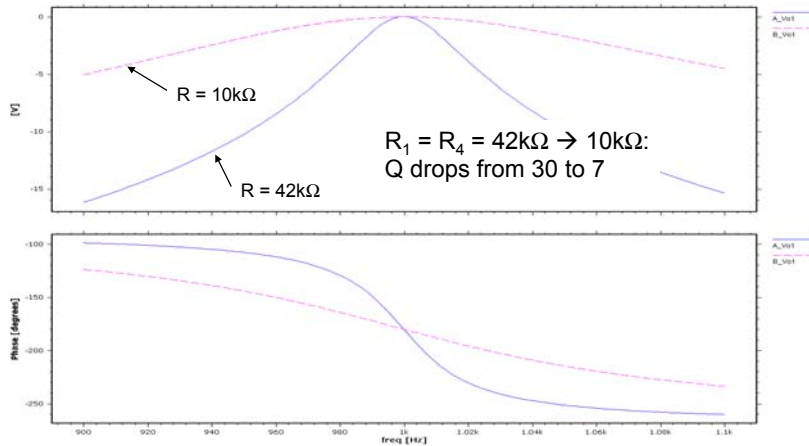

Noise versus Pole Q

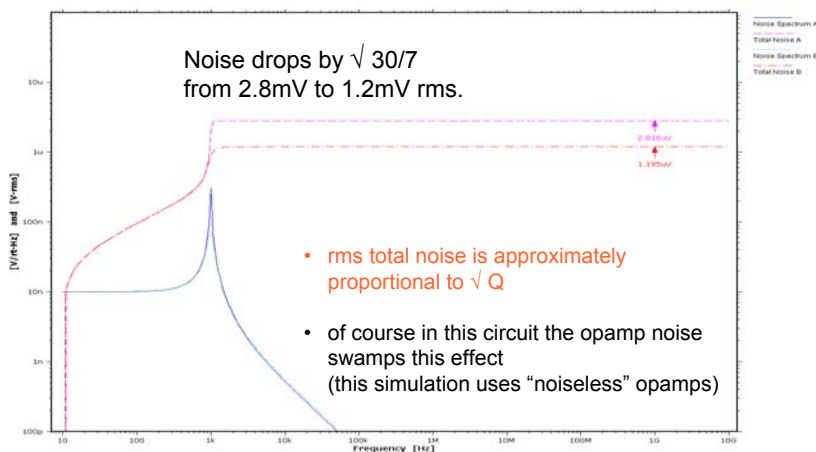

- rms total noise is approximately proportional to \sqrt{Q}
- of course in this circuit the opamp noise swamps this effect (this simulation uses "noiseless" opamps)

Noise Summary

- Thermal noise is a fundamental property of (electronic) circuits
- Noise is closely related to
 - Capacitor size and
 - Power dissipation
- In filters, noise is proportional to order, Q , and depends on implementation
- Operational amplifiers can contribute significantly to overall filter noise